

Will It Work?



Take a look at these circuit diagrams.
Which will work? Which need repairs?

Circle whether the bulb will be on or off. If you think the bulb will be off, provide an explanation on how the circuit can be repaired so that it will light.

Bulb On Bulb Off	Bulb On Bulb Off	Bulb On Bulb Off
Bulb On Bulb Off	Bulb On Bulb Off	Bulb On Bulb Off
Bulb On Bulb Off	Bulb On Bulb Off	Bulb On Bulb Off